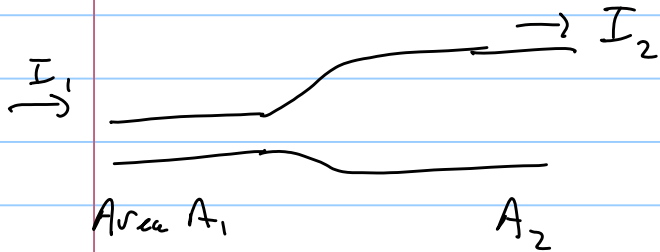


# Lecture 33 April 14

Note Title

4/14/2006




$$I = \int J dA = JA$$


$$J_1 A_1 = J_2 A_2$$

~~$$J_1 A_1 = J_2 A_2$$~~

$$v_{d_2} = v_{d_1} \frac{A_1}{A_2} \quad \text{incompressible flow} \\ \text{(edge } H_2O \text{ in pipe)}$$

Film loop

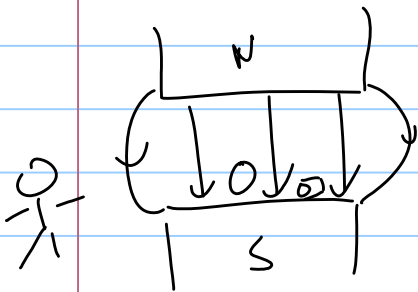

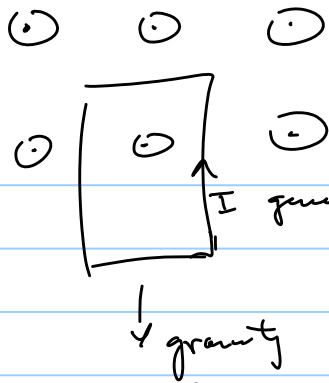

$I$  generates a  $B \Rightarrow$  change  $\Phi_B \Rightarrow$  another emf beyond that of the static field

We account for this effect by cal  $\Phi$  due to current  $\propto i$

$$\Phi = L i$$


$\uparrow$  inductance (self) internal flux

$\uparrow$  current in circuit

$$\text{Emf}_{\text{self}} = - \frac{d\Phi}{dt} = -L \frac{di}{dt}$$

$\uparrow$  assumed constant

Mutual inductor  $\rightarrow$

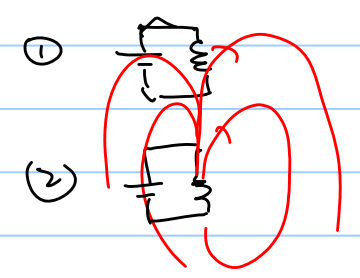


$$\Phi_{(1)} = M_{12} I_{(2)}$$

$\uparrow$  due to external flux

$\checkmark$  mutual inductor

Ex:

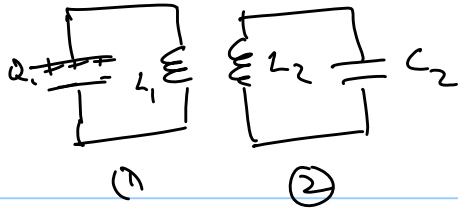

$$\textcircled{1} \sum_i V_i = 0$$

$$\left. \begin{aligned} \frac{Q_1}{C_1} - L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} &= 0 \\ \frac{Q_2}{C_2} - L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} &= 0 \end{aligned} \right\} \begin{array}{l} 2 \text{ coupled} \\ \text{ODE's} \end{array}$$

$$i_1 \neq \dot{Q}_1 \quad i_1 = -\frac{dQ_1}{dt} \quad i_2 = -\frac{dQ_2}{dt}$$

$$Q_1(t) = A \sin(\omega_N t + \alpha) \quad Q_2(t) = B \sin(\omega_N t + \alpha)$$

$$\omega_N = \frac{\omega_0}{\sqrt{1+K}}$$

$$\omega_0^2 = \frac{1}{L_1 C_1} = \frac{1}{L_2 C_2} \quad \text{let } k = \frac{M^2}{L_1 L_2}$$

Normal modes

